
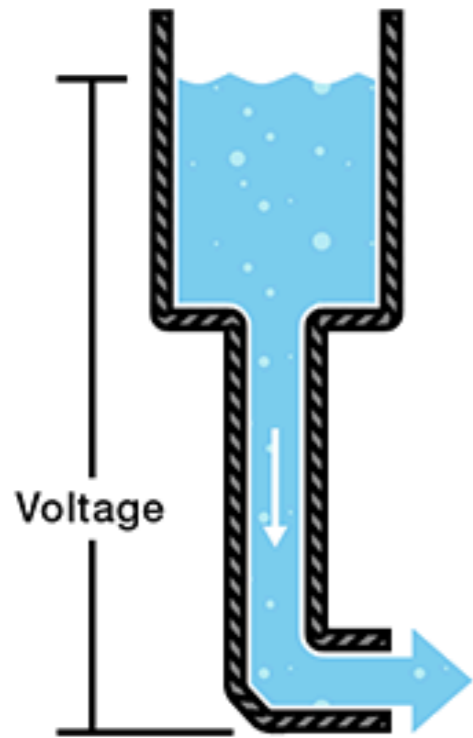


Physical Computing 2020

Luke Franzke, Florian Bruggisser

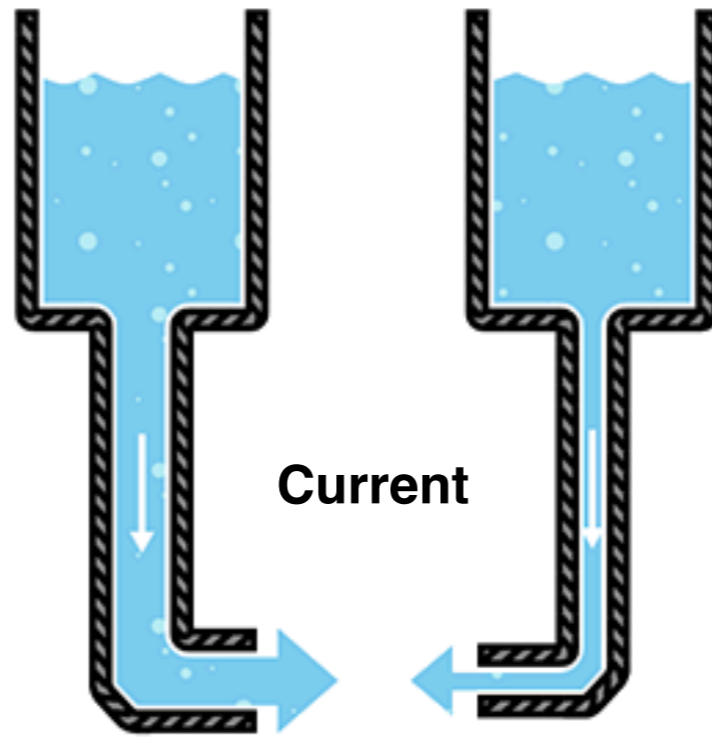

Spannung




Current

More

Less

Strom

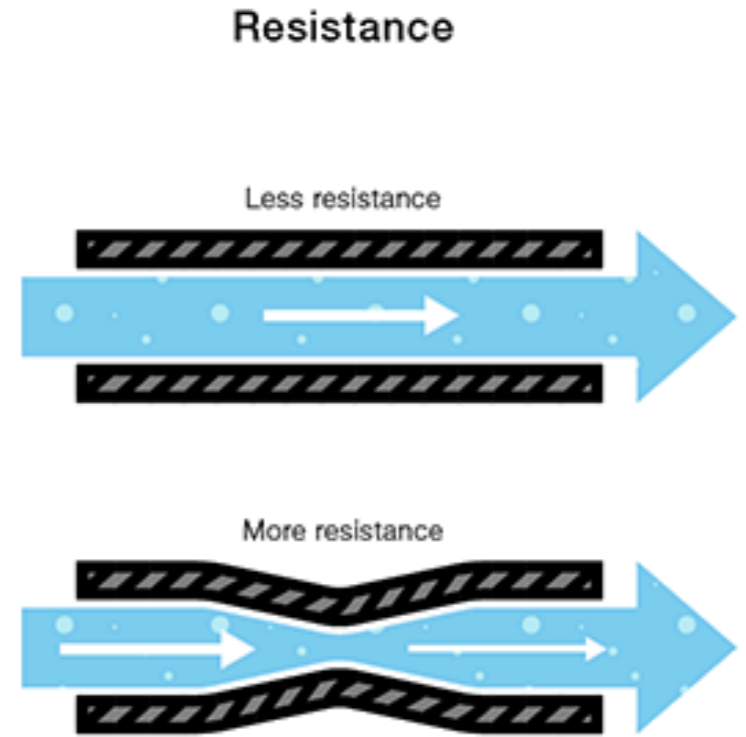


Resistance

Less resistance


More resistance

Widerstand

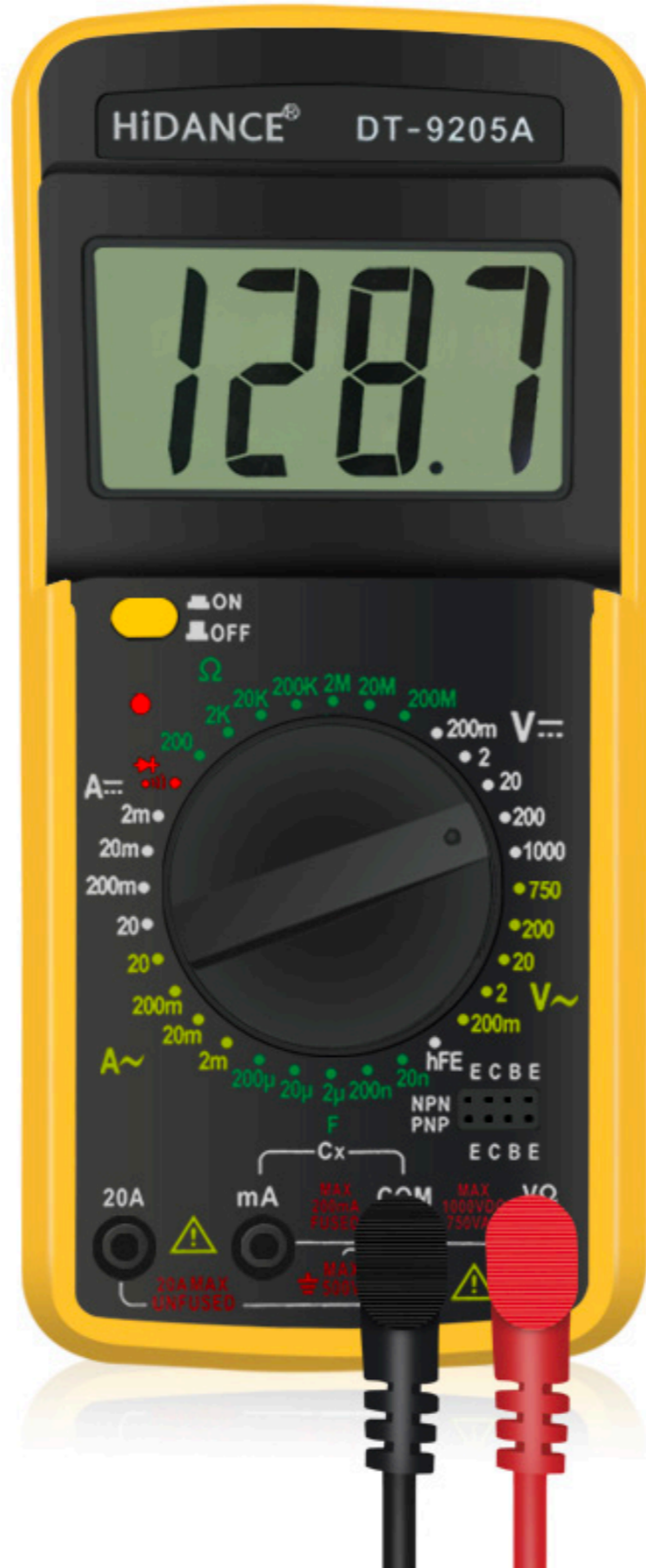


The multimeter is an essential tool for problem solving in electronics!


The Multimeter

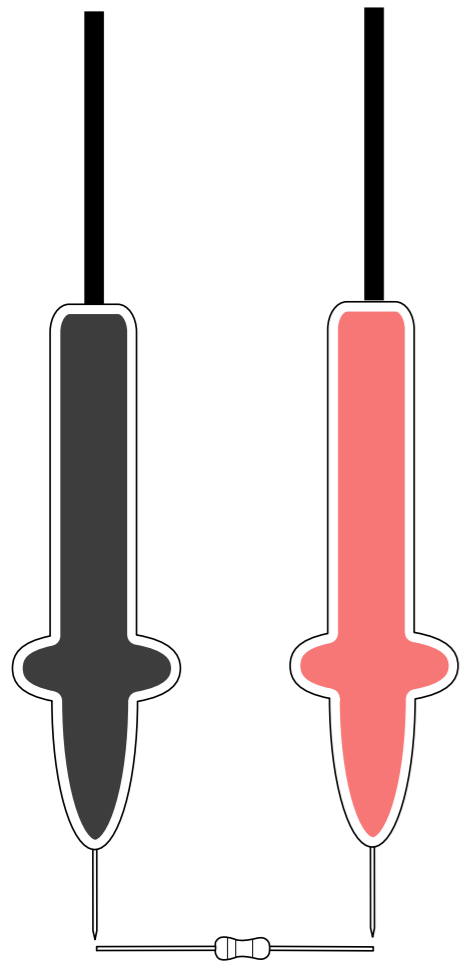

Resistance

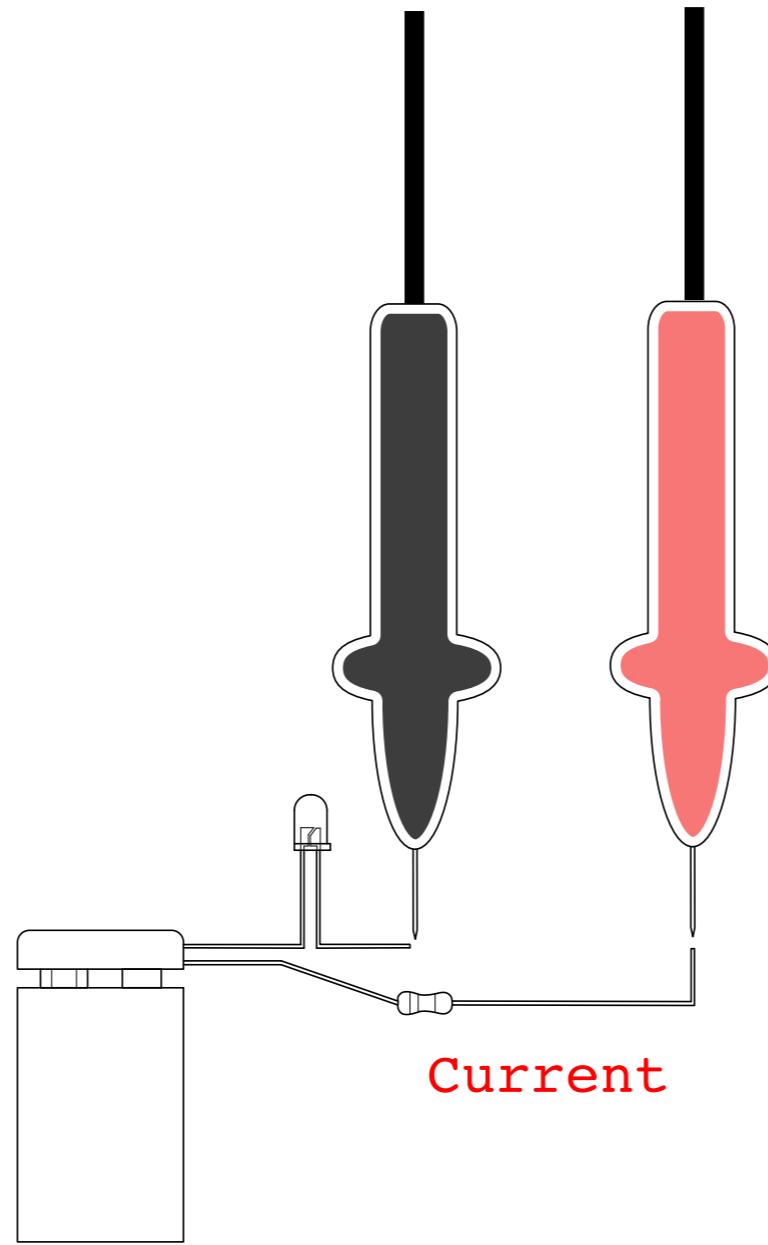



Current

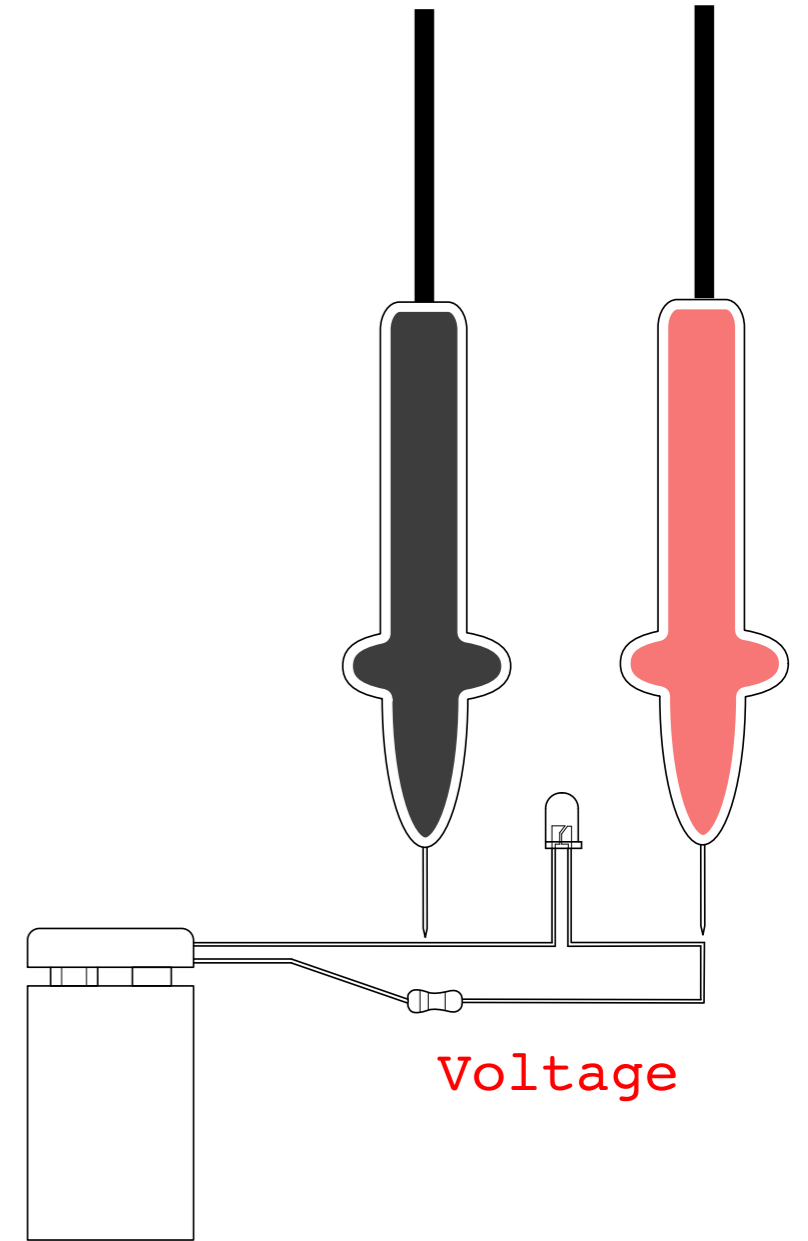

Voltage

The way we use the probes on a multimeter depends on what we are testing! Resistance of components should (ideally) be tested outside its circuit. For current we have to break the circuit, and insert the probes to close it again. Voltage, however, can be measure between any two points.

The Multimeter

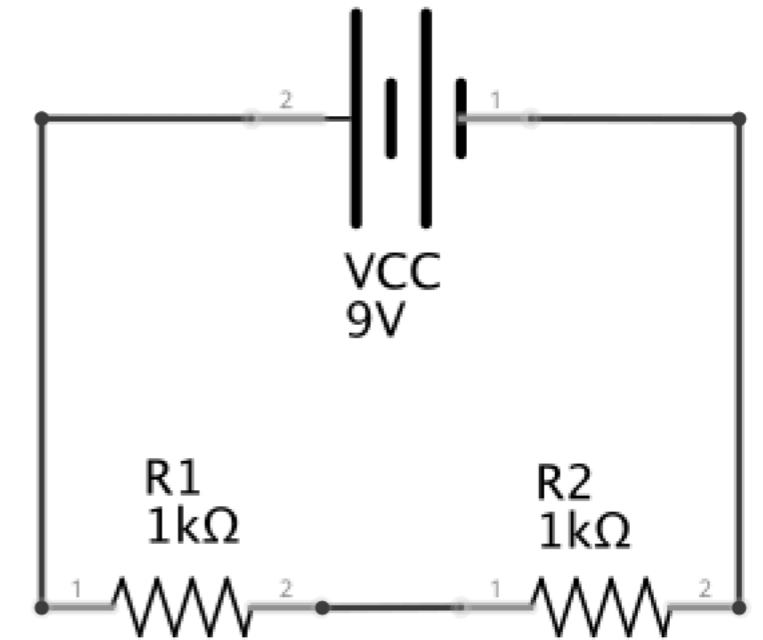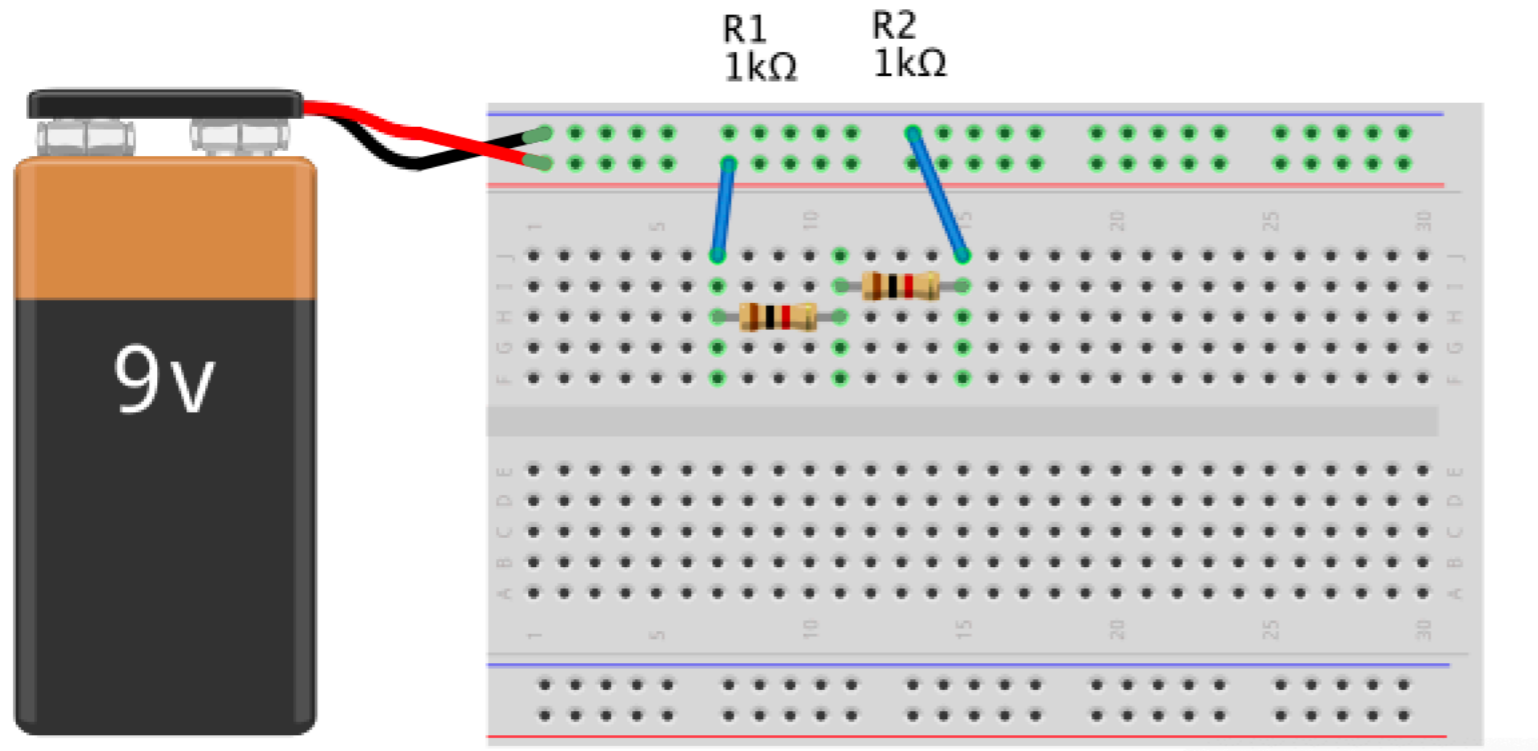


Exercise 3.1: Voltage Divider

Assembly the circuit with resistors of two different values. Try calculating the voltage between your resistors, and check with the multimeter if it's correct.

$$V_{res} = V_{cc} \times \frac{R_2}{(R_1 + R_2)}$$

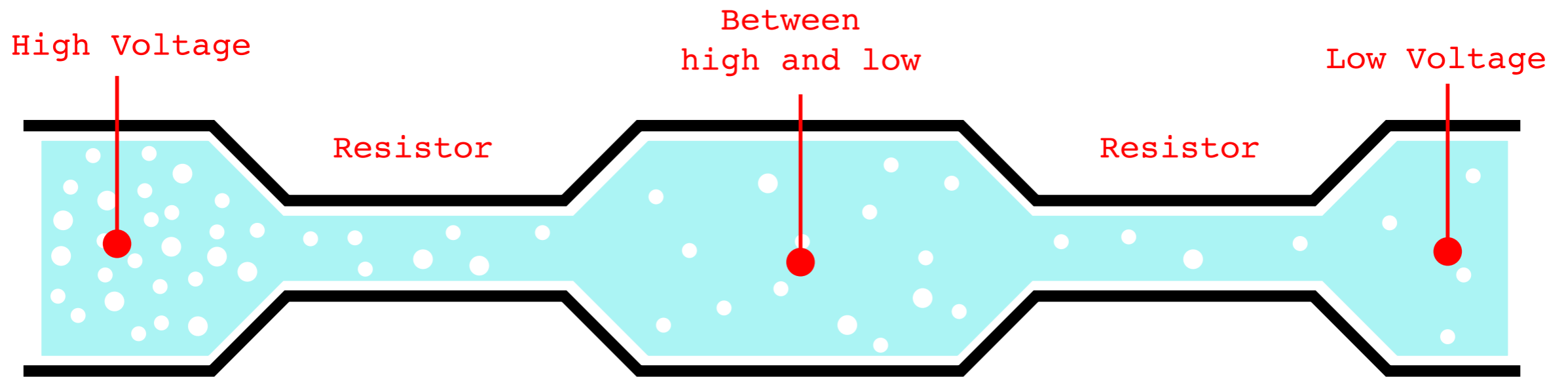
- V_{res} = resulting voltage
- V_{cc} = applied voltage (9V)
- R₁ = first resistor (1000 ohm)
- R₂ = second resistor (1000 ohm)



Voltage will drop when current flow through any component that converts electricity to some other form of energy.

Voltage Divider

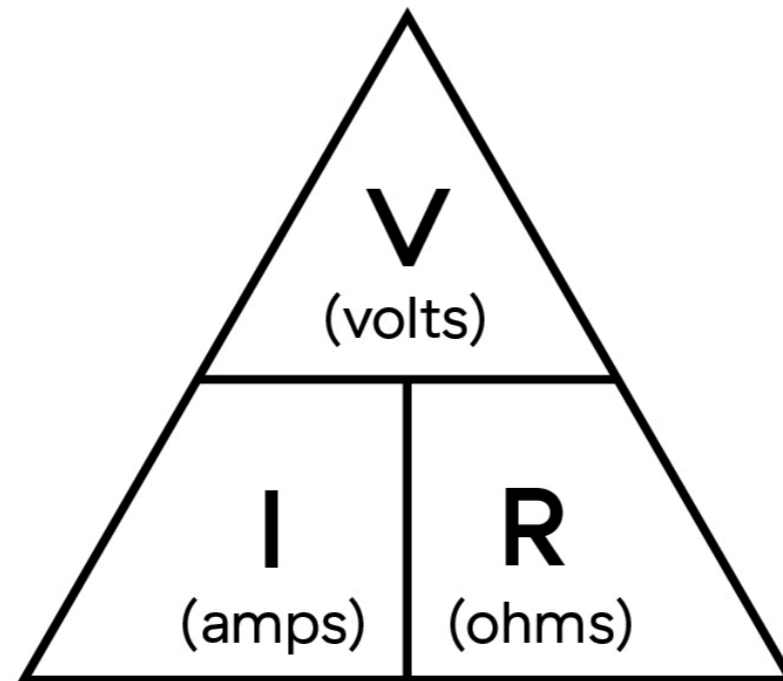There is an intrinsic relationship between voltage, current and resistance, expressed as ohms Law. We can use this formula to deduct the values in many situations




$$V = I \times R$$


$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

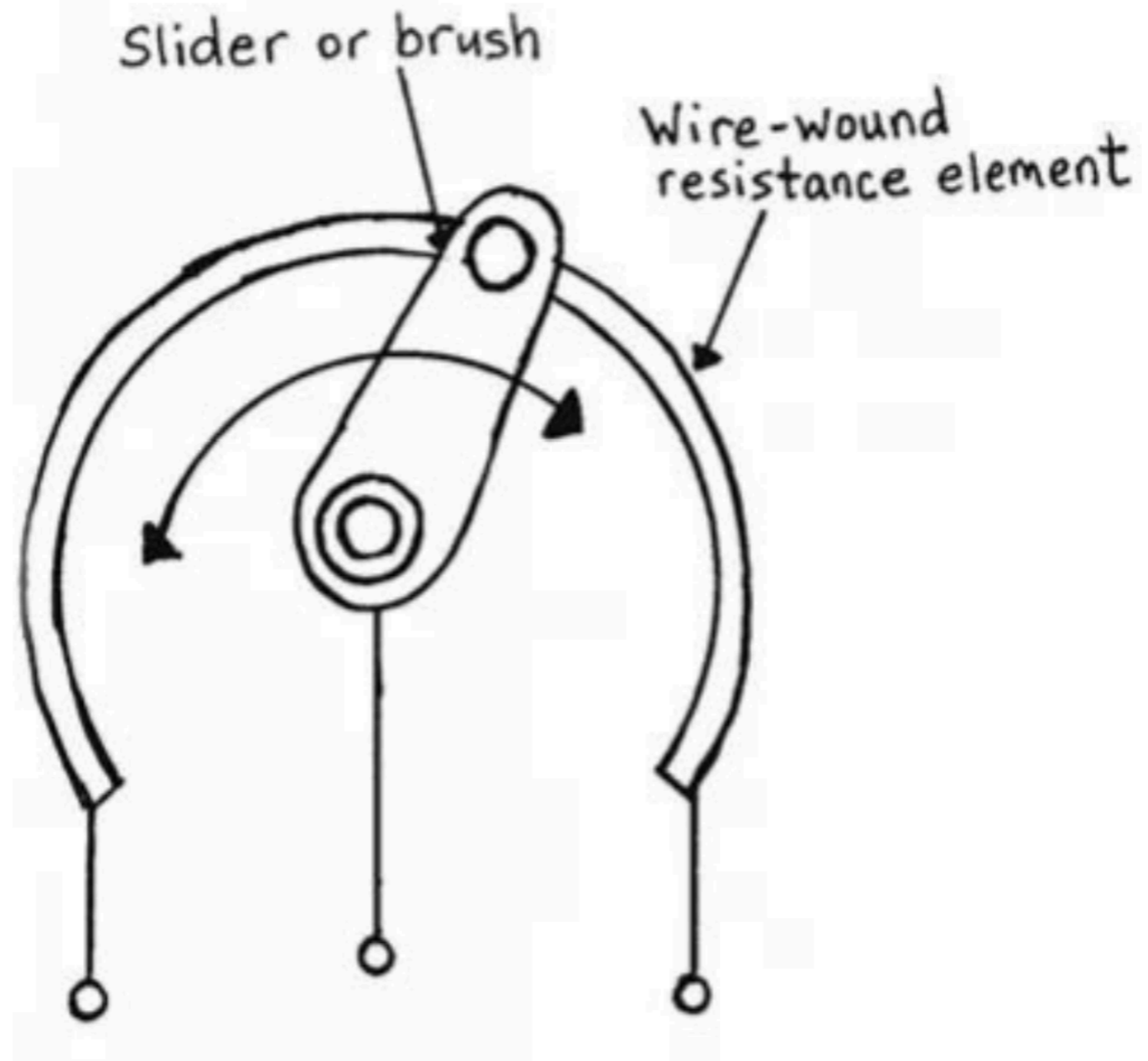A Potentiometer is also a voltage divider!



Potentiometer

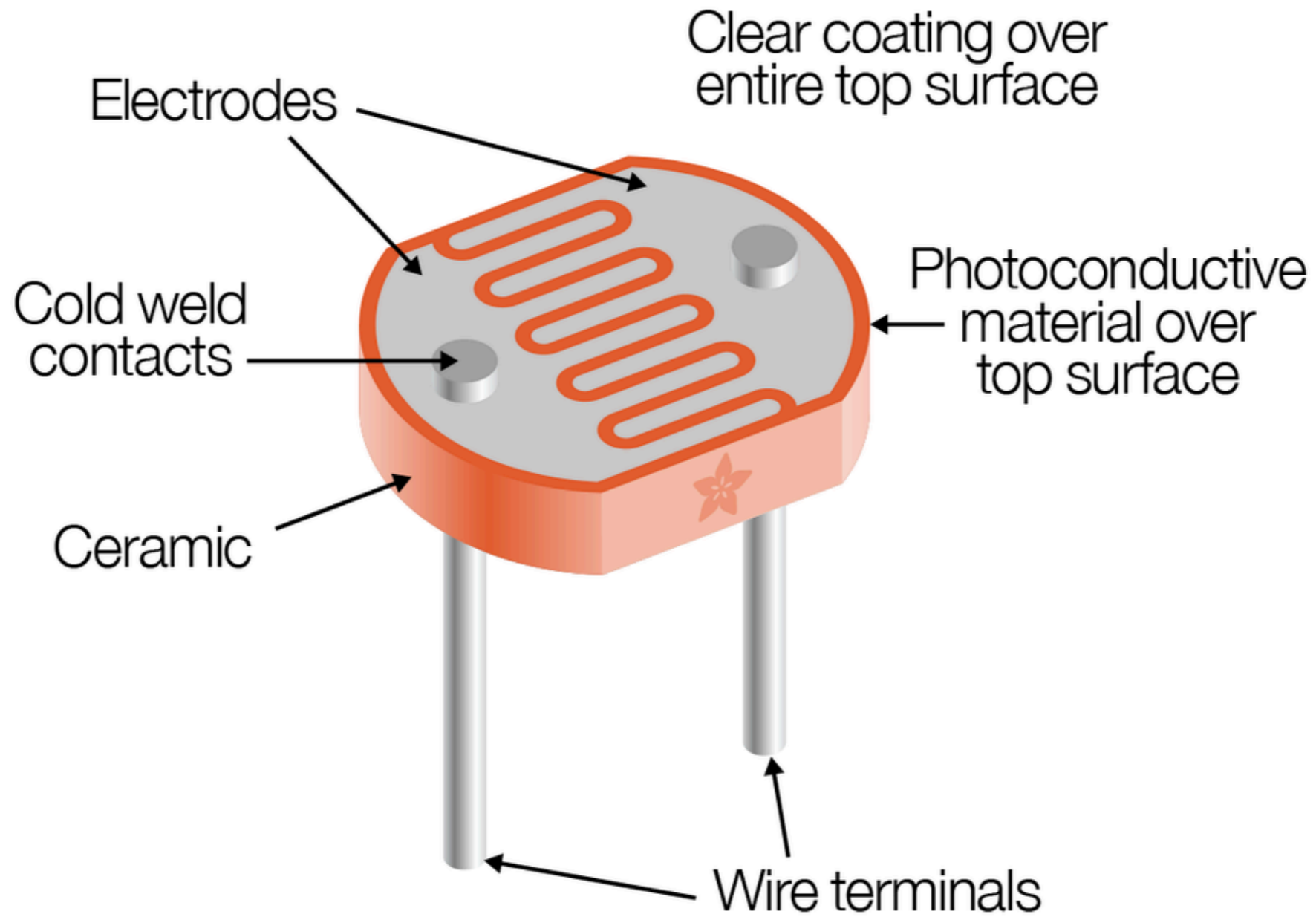


Analog Sensors

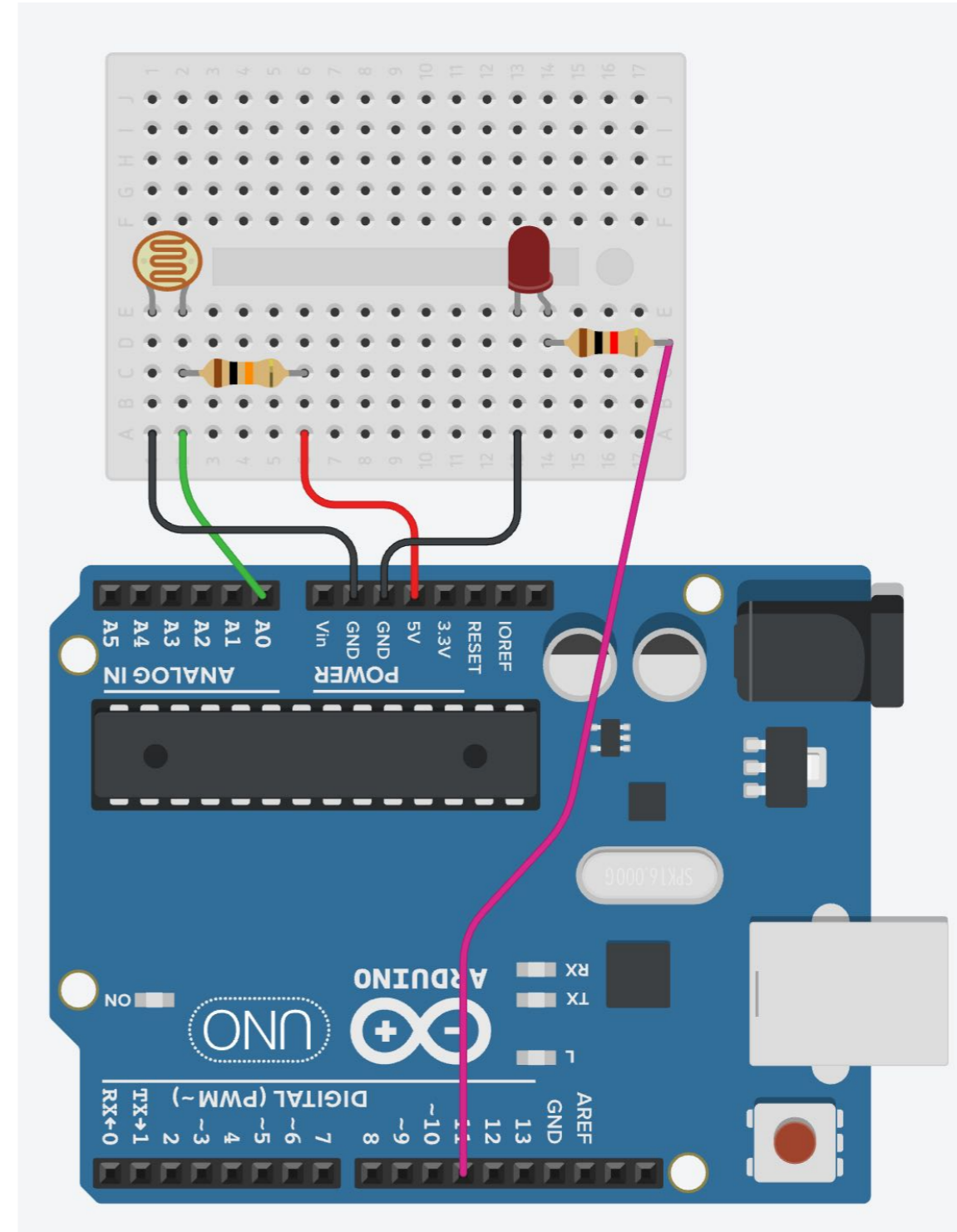
Exercise 3.2: Light Sensor

Build a circuit and code it to turn on an LED when it gets dark using a Photoresistor.



Optional: code it so the LED fades smoothly between Dark and light states.




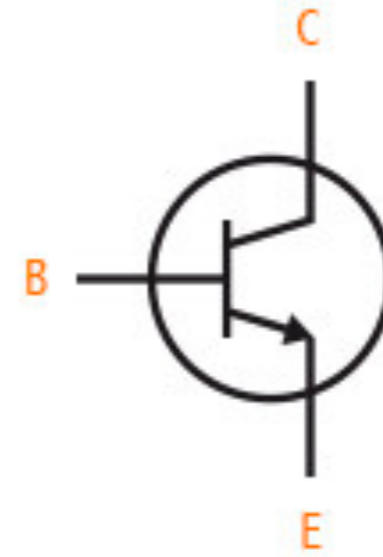To power loads greater than the 40mA our Arduino digital pins can provide, we need to use a transistor.



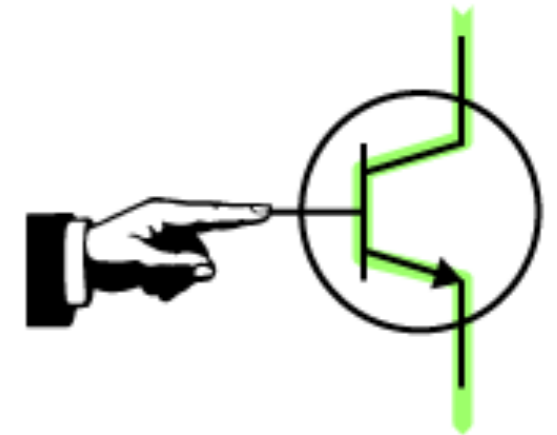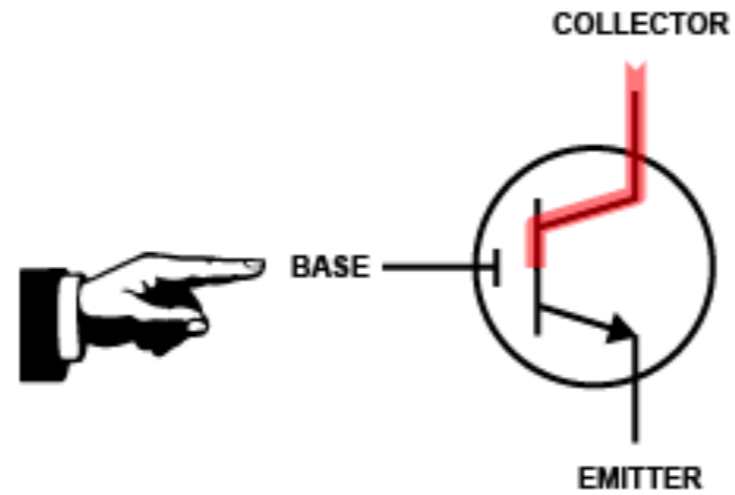
Transistors work like buttons, with a very small current on the base pin, allowing a larger current to flow between collector and emitter.



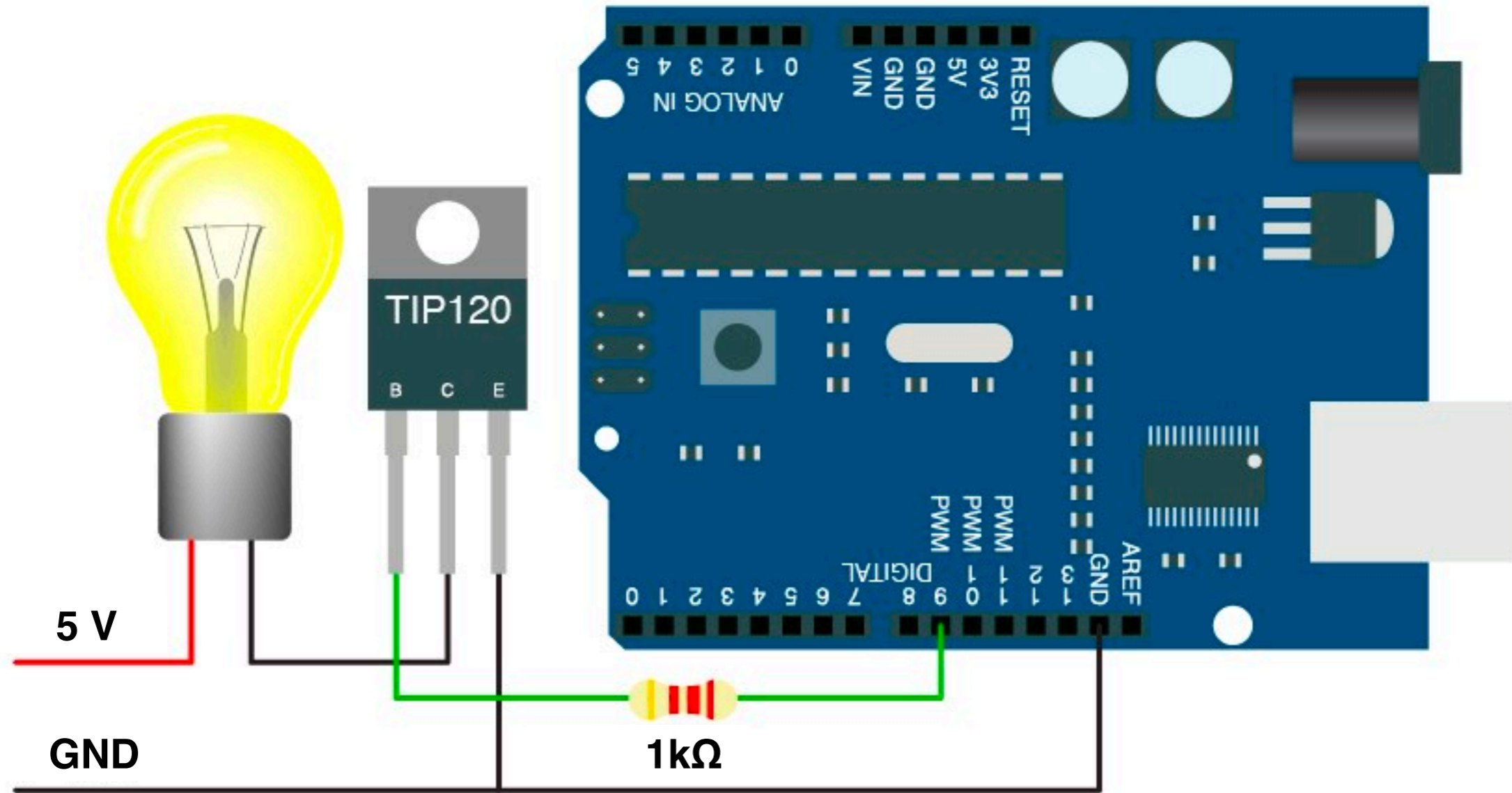


Transistors

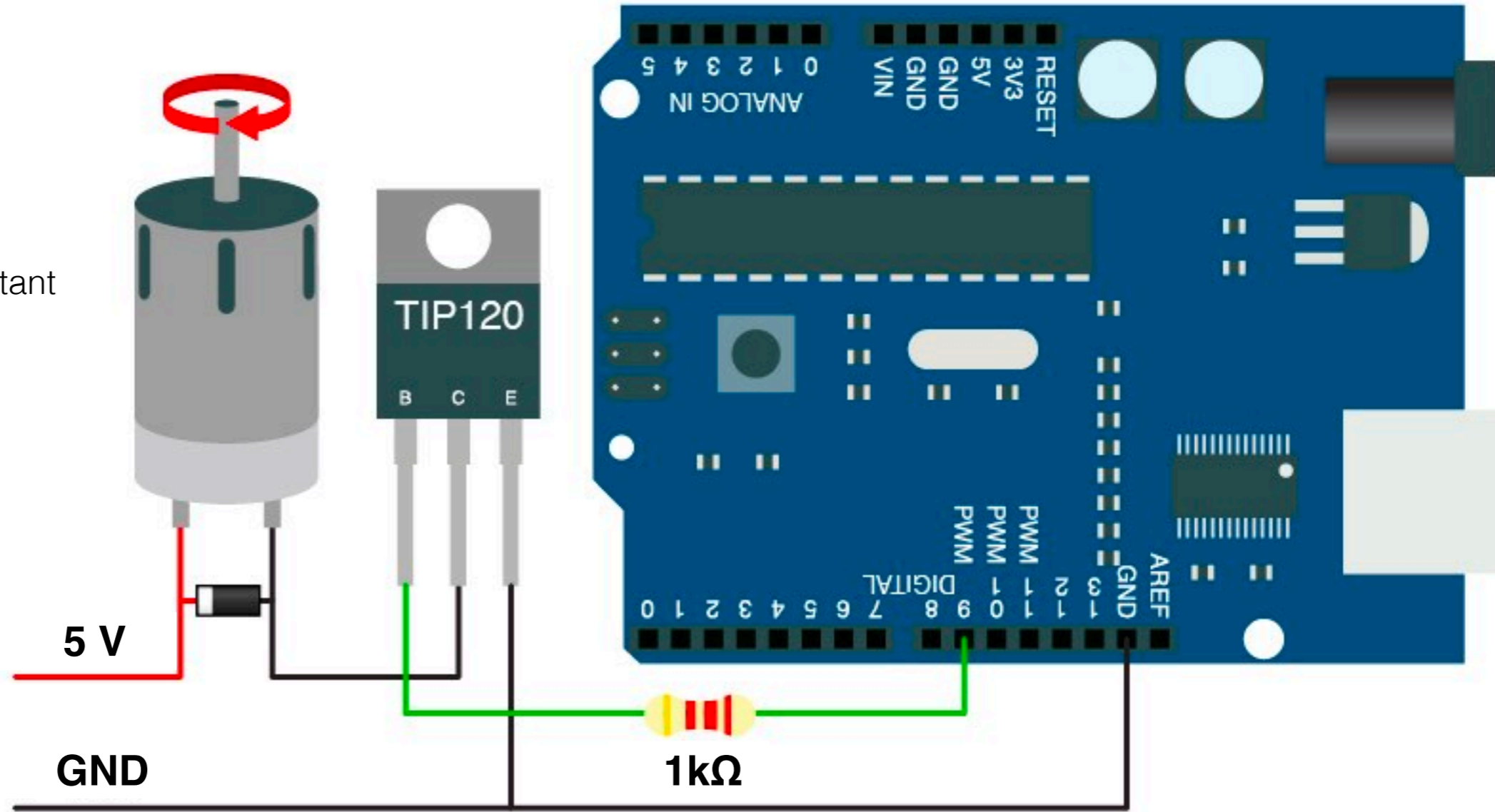Adding diode is important for inductive loads (motors for example)




Transistors


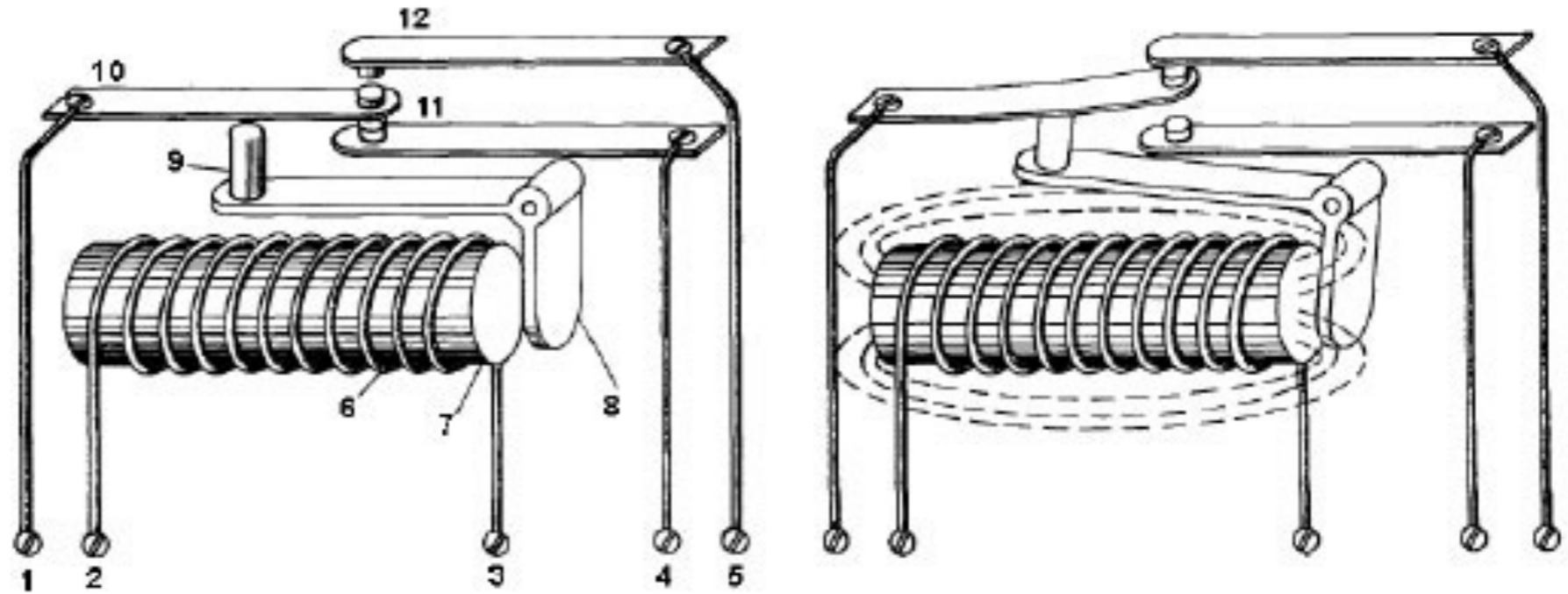
Relays can sometimes be used instead of transistors (for controlling very high loads, or when the HV circuits need to be completely isolated. But, they are loud and slow!



Relays

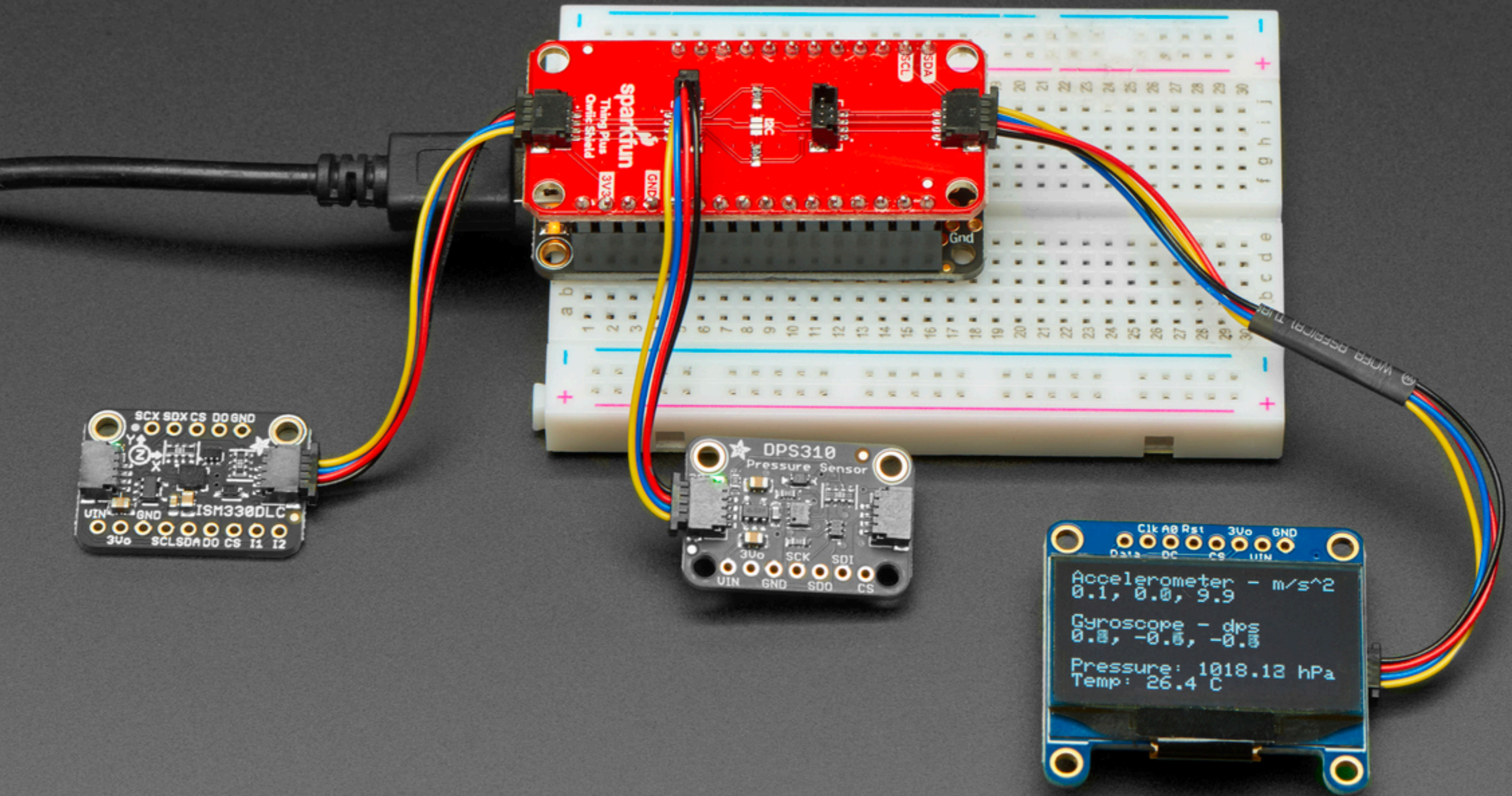


Digital Peripherals and Protocols

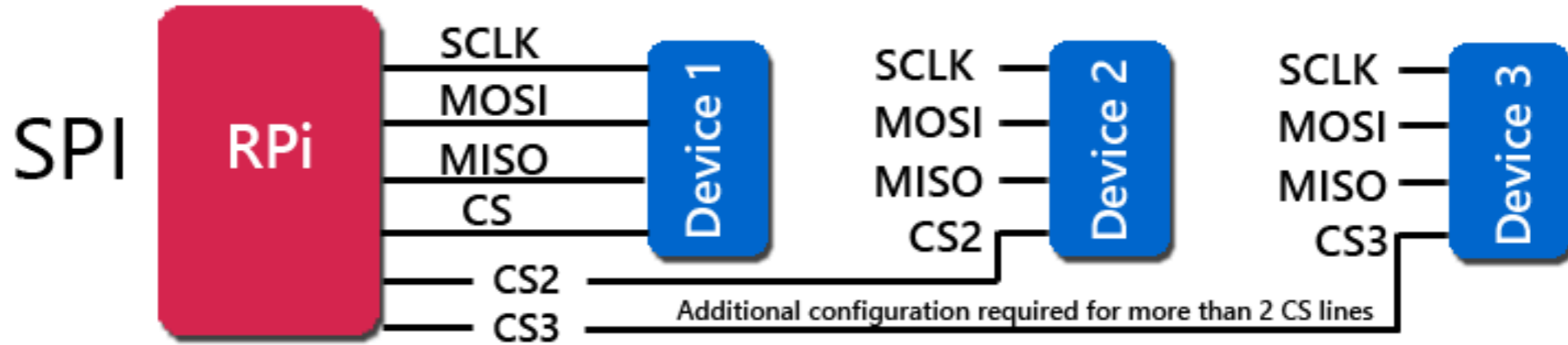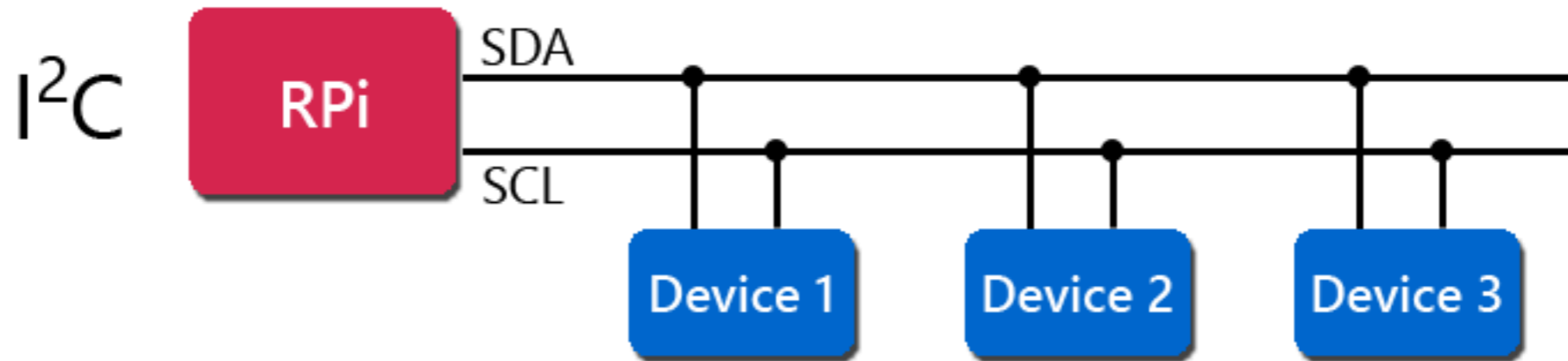

MBTechWorks.com


UART is useful for:

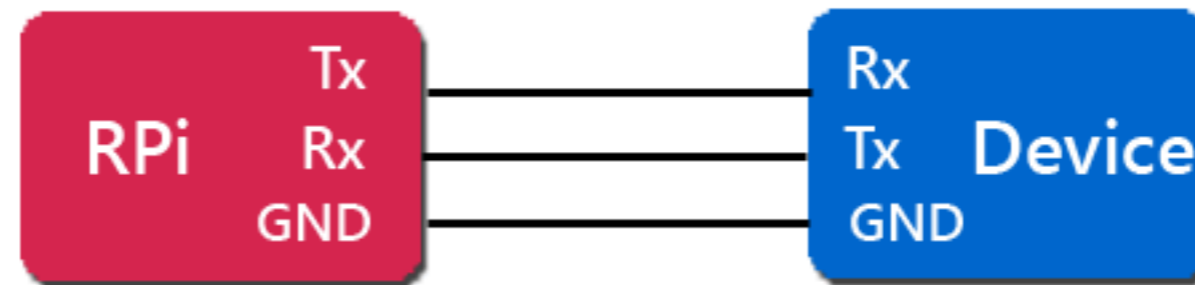- Communicating between Arduino and a Computer
- Communicating between two Arduino
- Communicating over longer distances




MBTechWorks.com

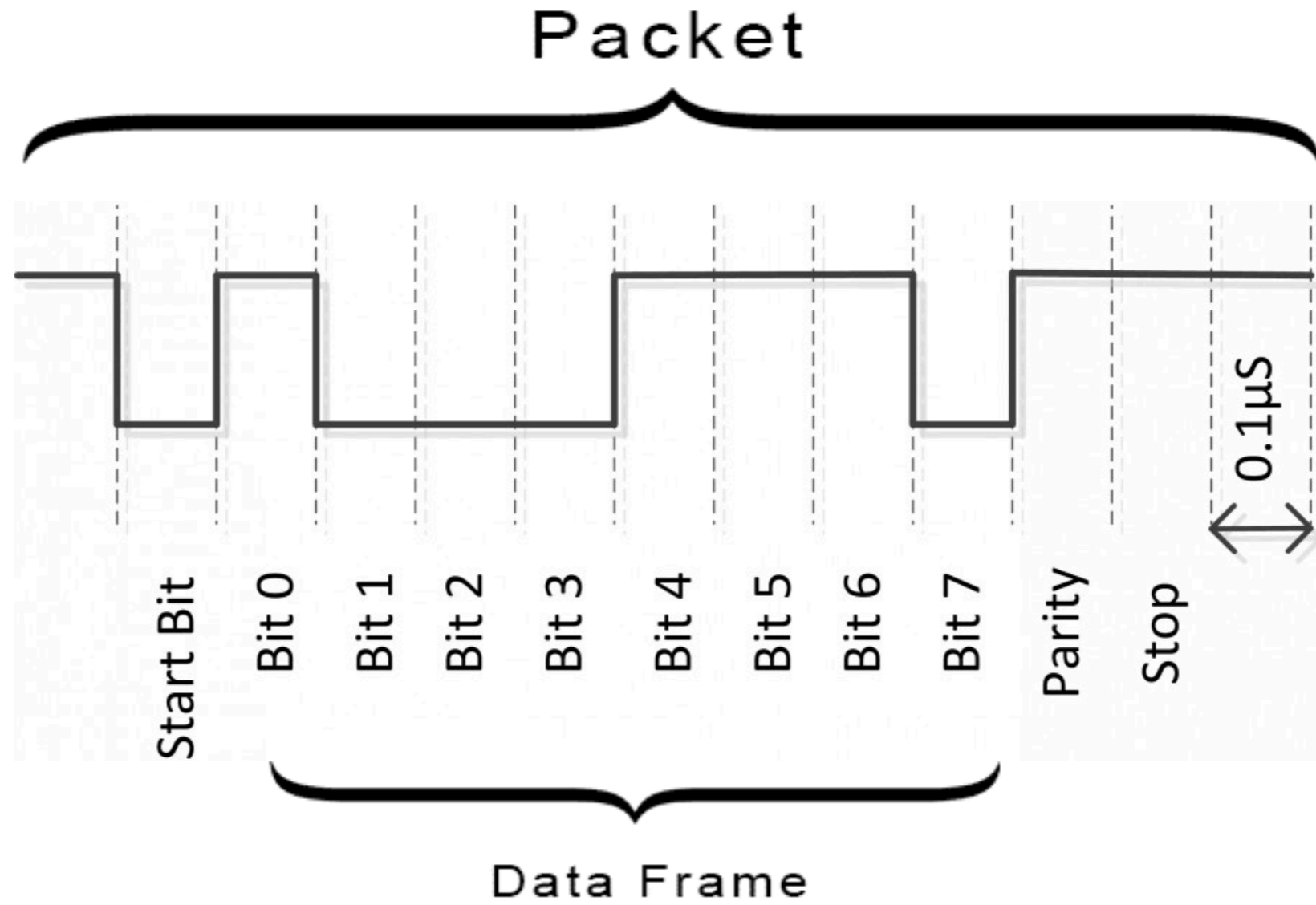UART - Universal Asynchronous Receiver/Transmitter



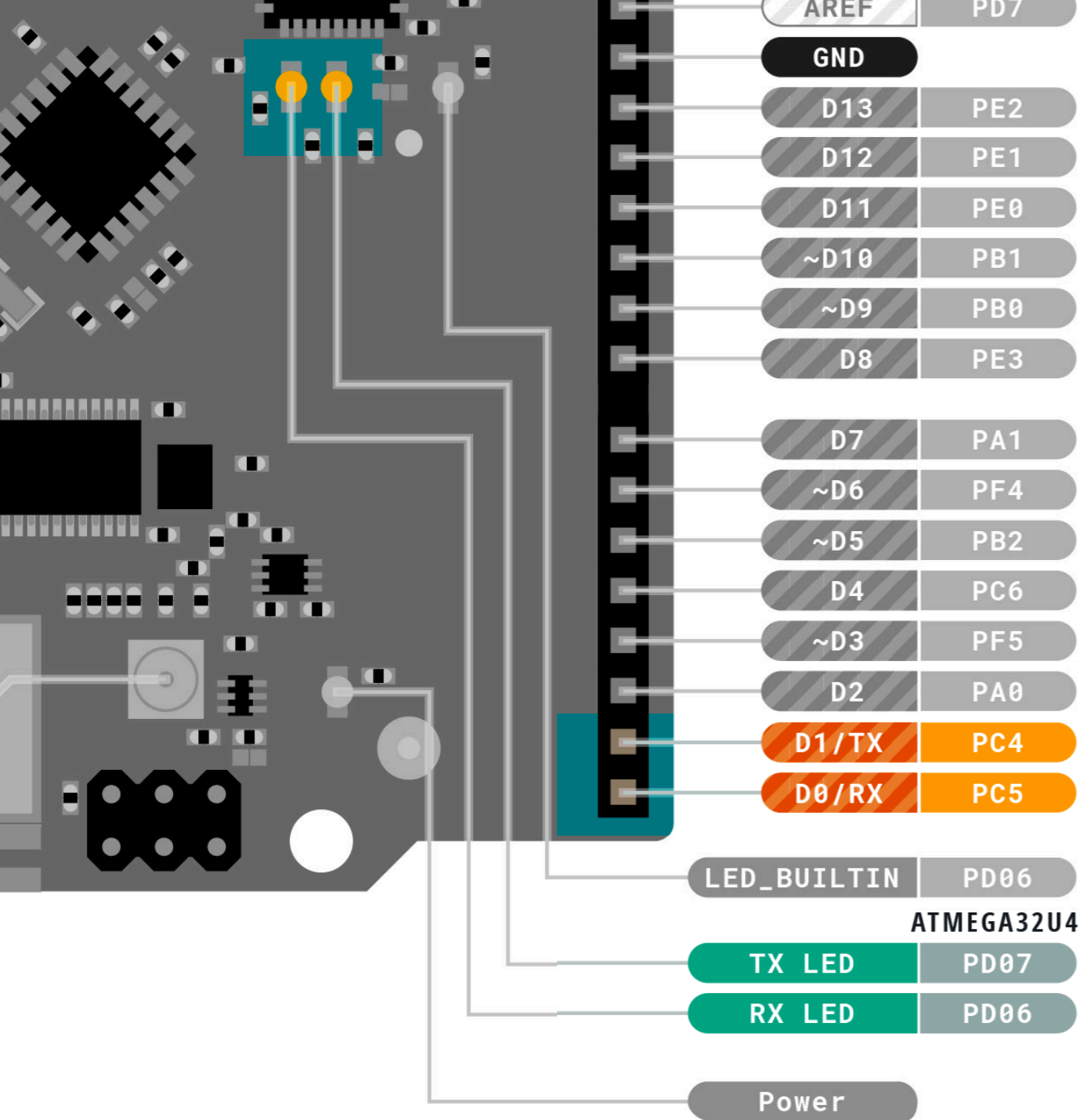
Universal Asynchronous Receiver/Transmitter.



```
Serial.begin(9600);
```

```
Serial.println("Hello World");
```

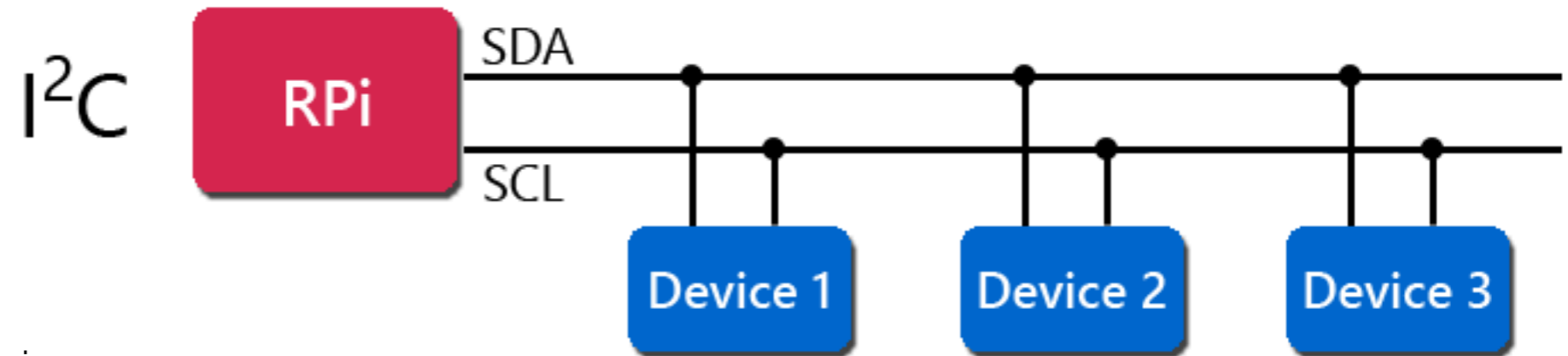UART - Universal Asynchronous Receiver/Transmitter




Uses:

- Communicating between Arduino and other chips (sensors or displays for example)
- Communicating between several Arduino boards on a small network


Limits:

- Fairly slow (probably doesn't matter for our project)
- I²C only works over short distances.


I²C (Inter Integrated Circuit)

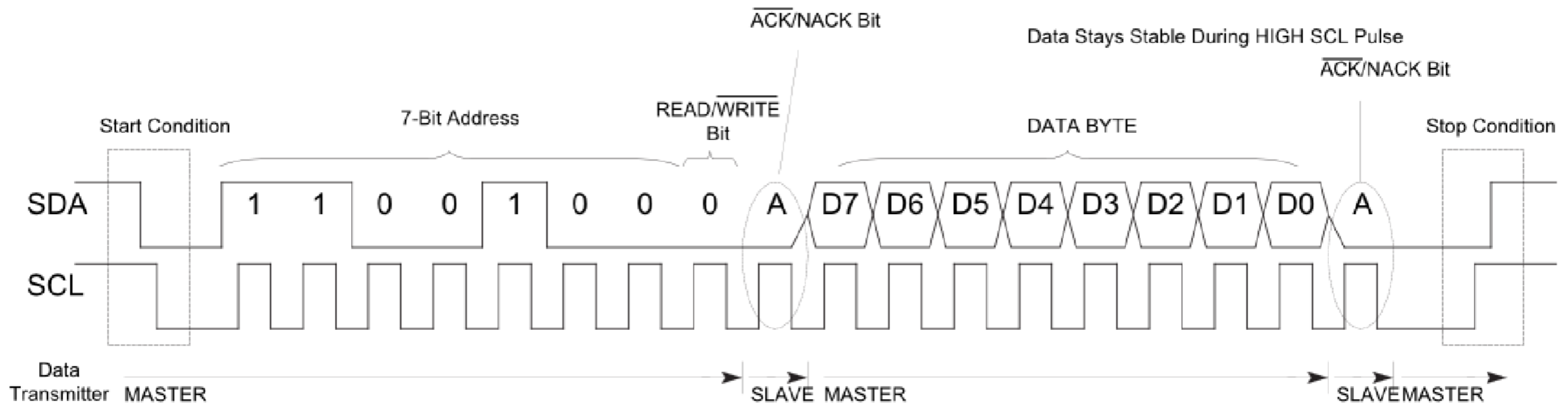

I²C (Inter Integrated Circuit)

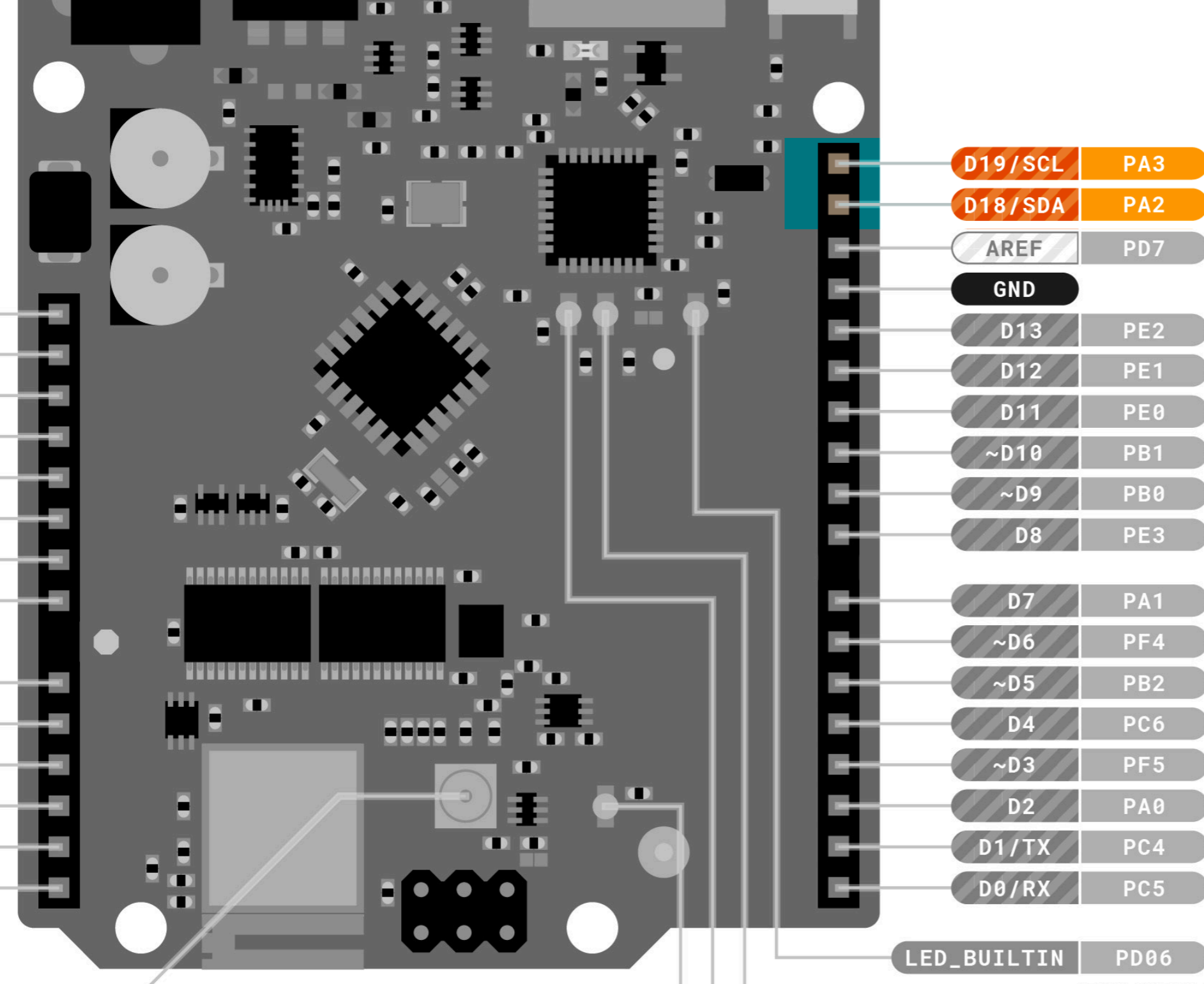


I²C (Inter Integrated Circuit)

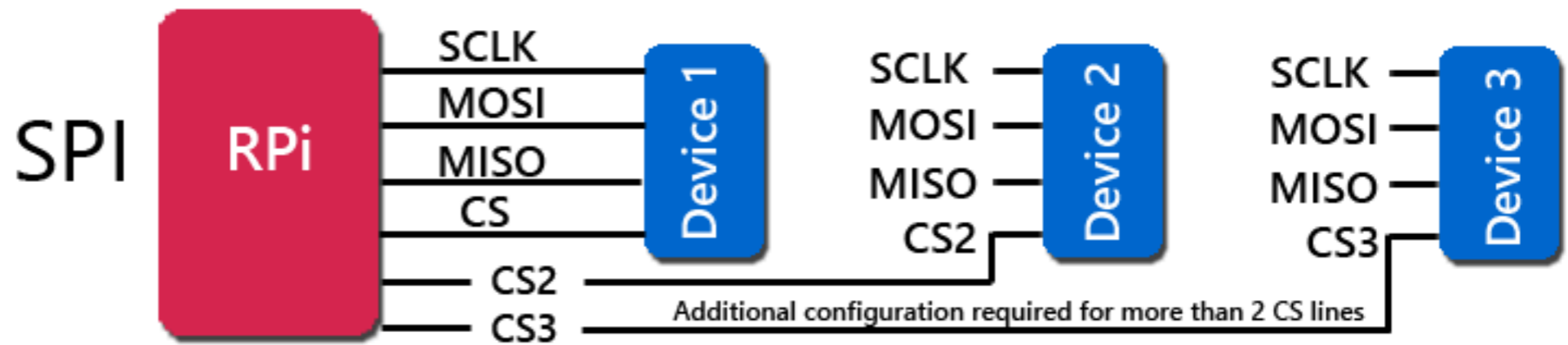

Much faster than I2c

Picking which device is in use is very simple, but wiring gets complicated if you have many slave devices.

SPI (Serial Peripheral Interface)

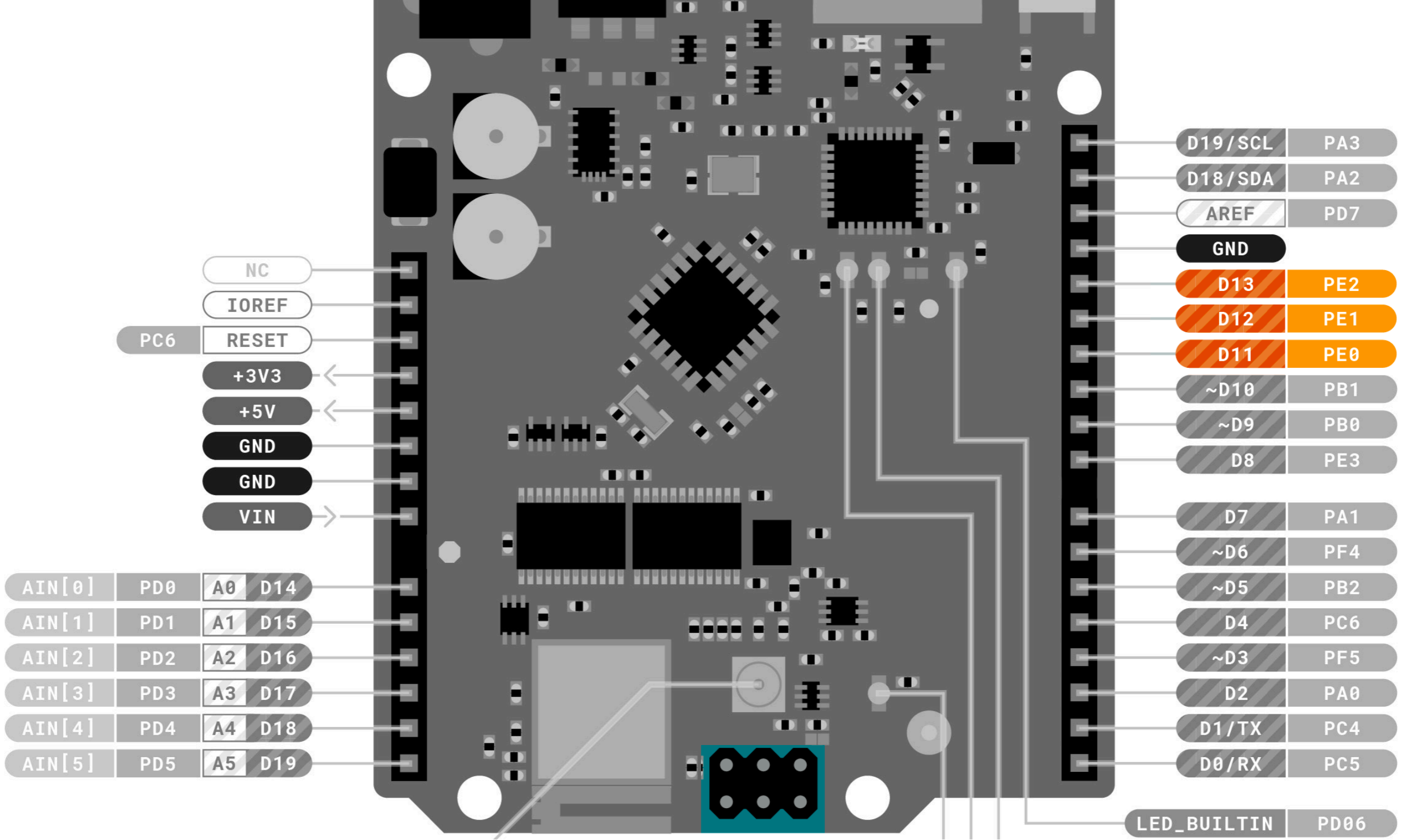

SPI (Serial Peripheral Interface)

Exercise 3.3: Reverse Parking helper

Using the VCNL 4040, build a circuit with at least 3 led's and code it show proximity level (i.e as an object moves closer, more led's turn on)

Alternative: Operate a motor so it “reverses” itself until it is too close to an object.



VCNL 4040

